



**SIDDARTHA INSTITUTE OF SCIENCE AND TECHNOLOGY: PUTTUR-517583
(AUTONOMOUS)**

QUESTION BANK (DESCRIPTIVE)

Subject with Code: Electronic Devices and Circuits (19EC0402) **Course & Branch:** B.Tech - EEE

Year & Sem: II-B.Tech & I-Sem

Regulation: R19

UNIT –I
PN JUNCTION DIODE

1. a) Define cut in voltage of a PN Junction diode and give its values for Si and Ge diodes. [L1][CO1][4M]
b) Illustrate the action of PN junction diode under forward bias and reverse bias and sketch its V-I Characteristics. [L2][CO1][6M]
2. a) Analyze the current components in a PN diode and determine the expression for diode current equation. [L4][CO1][6M]
b) When a reverse bias is applied to a germanium PN junction diode, the reverse saturation current at room temperature is $0.3\mu\text{A}$. Determine the current flowing in the diode when 0.15V forward bias is applied at room temperature. [L1][CO4][4M]
3. a) Solve the diode current for the forward bias voltage of 0.6V at 25°C , When the reverse saturation current of a silicon PN junction diode is $10\mu\text{A}$. [L3][CO4][4M]
b) Demonstrate the effect of temperature on V-I characteristics of PN junction diode. [L2][CO1][6M]
4. a) Construct the circuit symbol for the ideal diode characteristics. [L4][CO1][4M]
b) A p-n junction germanium diode has a reverse saturation current of $0.10\mu\text{A}$ at the room temperature of 27°C . It is observed to be $30\mu\text{A}$, when the room temperature is increased. Calculate the new room temperature. Also determine the current passing through the diode at this new temperature. [L3][CO4][6M]
5. a) Explain about Diode resistances and determine the expression for forward dynamic resistance. [L2][CO1][6M]
b) Determine the forward resistance of a PN junction diode when the forward current is 5mA at $T = 300\text{K}$. Assume Silicon diode. [L4][CO4][4M]
6. a) Define Transition and Diffusion capacitances of a PN Junction Diode. [L1][CO1][4M]
b) Determine the expression for transition capacitance of a PN Junction Diode. [L5][CO1][6M]
7. a) List the application of PN junction and Zener diodes. [L1][CO1][4M]
b) Determine the expression for Diffusion capacitance of a PN Junction Diode. [L5][CO1][6M]
8. a) Define Breakdown voltage and give the circuit symbol for Zener Diode. [L1][CO1][4M]
b) Discuss Breakdown mechanisms in PN Junction Diode. [L1][CO1][6M]
9. a) Define the importance of Diode Clipper and list its applications. [L1][CO1][4M]
b) Draw and explain the V-I characteristics of Zener diode. Show that the Zener diode can act as a voltage regulator with a neat diagram. [L1][CO5][6M]
10. a) Discuss the Positive and Negative Diode Clippers with neat waveforms. [L1][CO5][5M]
b) What is a Clamper circuit? Describe about positive and negative clampers with neat circuit diagrams. [L1][CO5][5M]

UNIT –II
RECTIFIERS, FILTERS AND SPECIAL PURPOSE DEVICES


1. a) Construct the circuit diagram of a Half wave rectifier and explain its operation with the help of i/p-o/p waveforms. [L2][CO1][5M]
b) Determine the expressions for Average DC current, Average DC Voltage, RMS Value of Current, DC Power Output and AC Power input of a Half Wave Rectifier. [L1][CO1][5M]
2. a) Construct the circuit diagram of a Full wave rectifier and explain its operation with the help of i/p- o/p waveforms. [L2][CO1][5M]
b) Determine the expressions for Average DC current, Average DC Voltage, RMS Value of Current, DC Power Output and AC Power input of a Full Wave Rectifier. [L1][CO1][5M]
3. a) A half wave rectifier is supplied from a 230V, 50 Hz supply with a step-down ratio of 3:1 to a resistive load of 10k Ω . The diode forward resistance is 75 Ω while transformer secondary is 10 Ω . Calculate maximum, average, RMS values of current, DC output voltage, efficiency of rectification and ripple factor. [L5][CO1][5M]
b) A full wave rectifier circuit is fed from a transformer having a center-tapped secondary winding. The rms voltage from either end of secondary to center tap is 30V. If the diode forward resistance is 2 Ω and that of the half secondary is 8 Ω , for a load of 1 K Ω , calculate DC power delivered to the load, efficiency of rectification and TUF of secondary. [L3][CO2][5M]
4. a) Construct a neat circuit diagram and waveforms, illustrate the construction and working of Bridge rectifier. [L2][CO1][5M]
b) A 5K Ω load is fed from a bridge rectifier connected across a transformer secondary whose primary is connected to 460V, 50 Hz supply. The ratio of number of primary turns to secondary turns is 2:1. Calculate dc load current, ripple voltage and PIV rating of diode. [L3][CO4][5M]
5. a) Construct the circuit diagram of Full wave rectifier with inductor filter and illustrate its operation. Also derive the expression for ripple factor. [L2][CO3][5M]
b) Calculate the value of inductance to be used in the inductor filter connected to a full wave rectifier operating at 60 Hz to provide a dc output with 4% ripple for a 100 Ω load. [L3][CO2][5M]
6. a) Construct neat circuit diagram and waveforms, discuss the operation of Full wave rectifier with capacitor Filter and determine the expression for its ripple factor. [L5][CO3][5M]
b) Calculate the value of capacitance to be used in a capacitor filter connected to a full wave rectifier operating at a standard aircraft power frequency of 400 Hz, if the ripple factor is 10% for a load of 500 Ω . [L3][CO2][5M]
7. a) Demonstrate the working principle of LC filter with neat diagram and derive the expression for its ripple factor. [L2][CO3][5M]
b) Discuss the construction and working principle of CLC or π section filter along with derivation for its ripple factor. [L3][CO2][5M]
8. a) Explain Liquid Crystal Display. Illustrate dynamic scattering LCD and field effect LCD with neat diagram. [L2][CO3][5M]
b) Discuss the construction, working principle and characteristics of LED with neat diagram. Also list the and applications of LED. [L3][CO2][5M]
9. a) Explain the principle involved in working of Varactor diode and give its characteristics. [L1][CO5][5M]
b) Sketch and explain the volt ampere characteristics of a Tunnel diode with the help of energy band diagrams. List the applications of tunnel diode. [L2][CO5][5M]
10. a) Demonstrate the construction, working and characteristics of UJT with neat diagram. [L2][CO5][5M]
b) Explain with diagram the construction, working and applications of Solar Cell. [L1][CO5][5M]

UNIT –III
TRANSISTOR CHARACTERISTICS: BJT & FET


1. a) Discuss the operation of NPN transistor with diagram. [L2][CO1][5M]
b) If the base current in a transistor is $20\mu\text{A}$ when the emitter current is 6.4mA , what are the values of α and β ? Also calculate the collector current. [L3][CO4][5M]
2. a) Give the current components of PNP transistor and explain the terms Emitter Efficiency, Base Transportation Factor and Large signal current gain. [L1][CO1][5M]
b) With neat diagram, explain the Input and Output characteristics of a BJT in CB Configuration. [L2][CO5][5M]
3. Discuss the Input and Output characteristics of a BJT in CE Configuration. Indicate the regions of operations in the output characteristics and list the applications in those regions. [L2][CO5][10M]
4. a) Describe the Input and Output characteristics of BJT in CC Configuration. [L2][CO5][6M]
b) Explain how a transistor acts as an amplifier with neat diagram? [L2][CO1][4M]
5. a) Derive the relation between α , β and γ of a Transistor. [L1][CO1][5M]
b) For a transistor, the leakage current is $0.1\mu\text{A}$ in CB configuration, while it is $19\mu\text{A}$ in CE configuration. Calculate α & β of the same transistor? [L3][CO4][5M]
6. Describe the construction and working principle of N-channel JFET. [L2][CO1][10M]
7. a) Define the JFET Volt-Ampere Characteristics and determine FET parameters. [L1][CO1][5M]
b) Compare the performance of BJT with FET. [L3][CO1][5M]
8. a) Explain the operation and characteristics of n-channel enhancement type MOSFET with the help of a neat diagram . [L2][CO5][8M]
b) List the differences between depletion and enhancement MOSFET. [L3][CO1][2M]
9. Discuss the operation and characteristics of n-channel depletion type MOSFET with diagram. [L2][CO5][10M]
10. a) Compare the performance of JFET with MOSFET. [L3][CO1][6M]
b) Mention the applications of JFET and MOSFET. [L1][CO1][4M]

UNIT- IV
TRANSISTOR BIASING AND THERMAL STABILIZATION

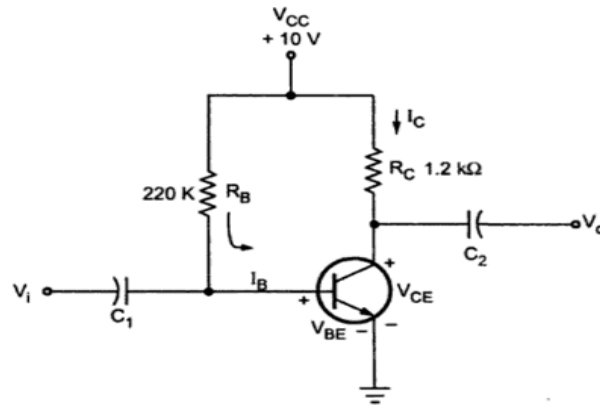
1. a) Define Transistor Biasing and explain the need for Biasing. [L1][CO3][5M]
 b) Explain the concept of DC and AC Load lines and discuss the criteria for fixing the Q-point. [L2][CO3][5M]
2. a) Mention different types of Biasing a Transistor and explain the Fixed Bias of a Transistor [L2][CO6][5M]
 b) Explain Collector to Base bias of a Transistor with neat circuit diagram. [L2][CO6][5M]
3. a) Determine the expressions for the stability factors S , S' and S'' of a BJT Fixed bias. [L3][CO3][8M]
 b) What are the disadvantages of fixed bias circuit of BJT? [L1][CO1][2M]
4. a) Define Stability Factor S . Derive the stability factor S for collector to base bias of BJT. [L3][CO6][5M]
 b) Design a collector to base bias circuit for the specified conditions: $V_{cc} = 15V$, $V_{CE} = 5V$, $I_C = 5mA$ and $\beta = 100$. [L6][CO2][5M]
5. Derive the stability factors S , S' and S'' of a BJT Voltage Divider bias. [L3][CO6][10M]
6. a) For the circuit shown in the Figure, calculate I_B , I_C , V_{CE} , V_B , V_C and V_{BC} . Assume that $V_{BE} = 0$ and $\beta = 50$. [L3][CO2][5M]



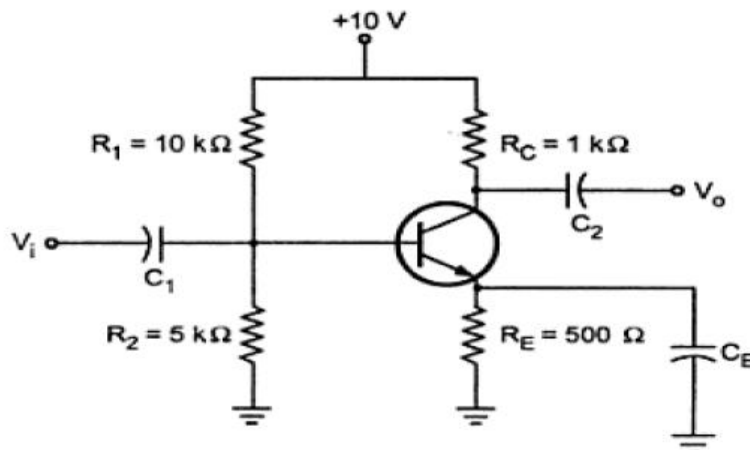- b) Discuss Diode Compensation Technique for the parameters V_{BE} and I_{CO} . [L2][CO3][5M]
7. a) Describe Thermistor Compensation Technique. [L1][CO3][4M]
 b) For the circuit shown in Fig. $\beta = 100$ for the silicon transistor. Calculate V_{CE} and I_C . [L3][CO2][5M]




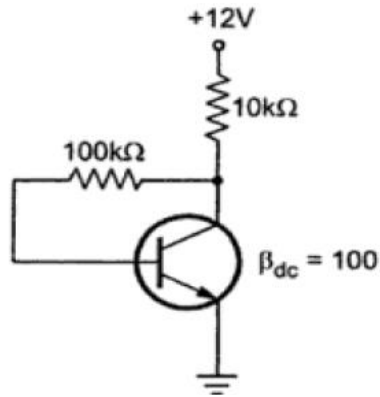8. a) Discuss about Thermal Runaway and Thermal Resistance. [L2][CO3][5M]
 b) Calculate the Q-point values for the circuit shown in the Fig. [L3][CO2][5M]



9. Draw the dc load line for the following transistor configuration. Obtain the quiescent Point.

[L3][CO2][10M]

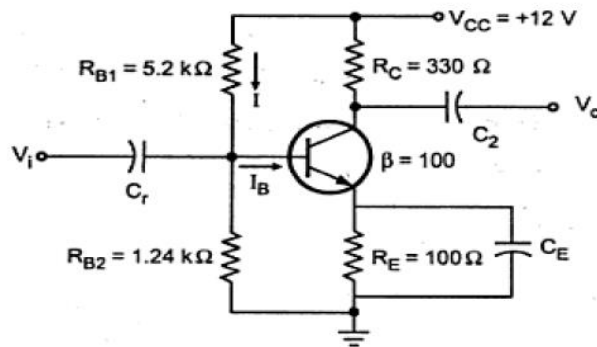

10. a) Describe Sensistor Compensation Technique.


[L1][CO3][4M]

b) Derive the condition for achieving Thermal Stability.


[L3][CO3][6M]

UNIT- V
SMALL SIGNAL LOW FREQUENCY TRANSISTOR AMPLIFIER

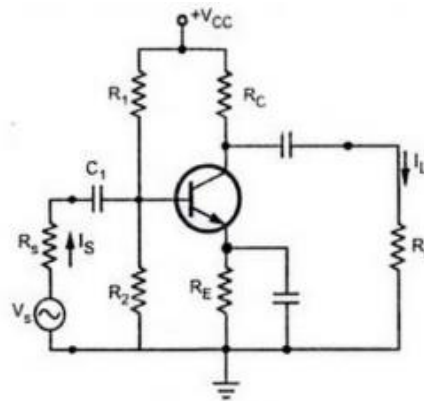1. a) Discuss the frequency response of an amplifier. [L2][CO1][4M]
 b) Why hybrid model is used for the analysis of BJT amplifier at low frequencies? Draw the hybrid model for CE transistor and derive the hybrid parameters. [L2][CO1][6M]
2. Applying low frequency h-parameter model, derive the expressions for voltage gain, current gain, input impedance and output admittance for a BJT Amplifier in CE configuration. [L3][CO3][10M]
3. a) Derive the parameters of CE amplifier using approximate analysis with a neat diagram. [L2][CO3][5M]
 b) Obtain the expressions for current gain, voltage gain, input impedance and output impedance of CB amplifier using simplified hybrid model. [L2][CO3][5M]
4. a) Determine the parameters A_i , R_i , A_v and R_0 of Common Collector Amplifier using simplified hybrid model analysis. [L3][CO3][5M]
 b) A voltage source of internal resistance, $R_s = 900\Omega$ drives a CC amplifier using load resistance $R_L = 2000\Omega$. The CE h parameters are $h_{fe} = 60$, $h_{ie} = 1200\Omega$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Compute A_i , R_i , A_v and R_0 using approximate analysis. [L3][CO2][5M]
5. A CE amplifier is driven by a voltage source of internal resistance $R_s = 800\Omega$ and the load impedance of $R_L = 1000\Omega$. The h-parameters are $h_{ie} = 1k$, $h_{fe} = 50$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Calculate current gain, voltage gain, input impedance and output impedance using exact analysis and approximate analysis. [L3][CO2][10M]
6. For a CB transistor amplifier driven by a voltage source of internal resistance $R_s = 1200\Omega$, the load Impedance of $R_L = 1000\Omega$. The h parameters are $h_{ib} = 22\Omega$, $h_{rb} = 3 \times 10^{-4}$, $h_{fb} = -0.98$, $h_{ob} = 0.5\mu A/V$. Calculate current gain, voltage gain, input impedance and output impedance using exact analysis and approximate analysis. [L3][CO2][10M]
7. Consider a single stage CE amplifier with $R_s = 1k\Omega$, $R_1 = 50k\Omega$, $R_2 = 2k\Omega$, $R_c = 1k\Omega$, $R_L = 1.2k\Omega$, $h_{fe} = 50$, $h_{ie} = 1.1k$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2.5 \times 10^{-4}$, as shown in Fig. Find A_i , R_i , A_v , A_{v_s} , A_{i_s} and R_0 . [L3][CO2][10M]



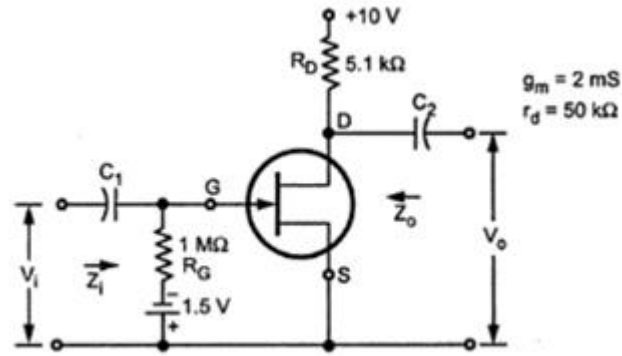8. a) Obtain the expression for current gain, voltage gain, input impedance and output impedance for Common Emitter Amplifier with Emitter Resistor using simplified hybrid model. [L2][CO3][5M]
 b) A CE amplifier is driven by a voltage source of internal resistance $R_s = 1000\Omega$ and the load impedance of $R_c = 2k\Omega$. The h-parameters are $h_{ie} = 1.3k$, $h_{fe} = 55$, $h_{oe} = 22\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Neglecting biasing resistors, compute current gain, voltage gain, input impedance, output impedance for the value of Emitter Resistor $R_E = 200\Omega$ inserted in the emitter circuit. [L3][CO2][5M]
9. a) For the circuit shown in Figure below, determine input impedance, output impedance and voltage gain. [L4][CO5][5M]



b) Sketch the circuit diagram of JFET Common Source amplifier with voltage divider bias for by passed R_s and determine the expression for input impedance, output impedance and voltage gain.

[L2][CO6][5M]

10. Derive the expressions for input impedance, output impedance and voltage gain of JFET Common Drain amplifier with neat diagram.

[L2][CO5][10M]