



**SIDDHARTH GROUP OF INSTITUTIONS::PUTTUR(A
UTONOMOUS)**

Siddharth Nagar, Narayanananam Road – 517583

QUESTIONBANK(DESCRIPTIVE)

Subject with Code: Power Electronics (19EE0210)

Course & Branch: B.Tech & EEE

Year & Sem: III-B.Tech & I-Sem

Regulation: R19

UNIT-I

POWER SWITCHING DEVICES

- 1) Explain the Types of Power Semiconductor Devices and Mention Advantages, Applications of Power Semi-Conductor Devices? [CO2,L2][10M]
- 2) a) Explain V-I Characteristics of Power Diode? [CO3,L2][5M]
- b) Necessity of Commutation, What are the Types of Commutation? [CO2,L2][5M]
- 3) Draw and explain V-I characteristics of SCR and Its working. [CO3,L4][10M]
- 4) Briefly explain about Insulated Gate Bipolar Transistor (IGBT) and its switching characteristics. [CO3,L2][10M]
- 5) Explain the Resistance firing circuit with the necessary waveforms. [CO2,L2][10M]
- 6) Briefly explain about Metal Oxide Semiconductor Field Effect Transistor (MOSFET) and its switching Characteristics. [CO3,L3][10M]
- 7) Explain briefly voltage commutation and Draw the output waveforms. [CO2,L2][10M]
- 8) Analyze the MOSFET using its output and transfer Characteristics. [CO3,L5][10M]
- 9) Explain briefly current commutation and Draw the output waveforms. [CO2,L2][10M]
- 10) A bipolar transistor has current gain $\beta = 40$. The load resistance $R_L = 10 \text{ ohm}$, dc supply voltage $V_{CC} = 130\text{v}$ and input voltage to base circuit $V_B = 10\text{v}$. For $V_{CES} = 1\text{v}$ and $V_{BES} = 1.5\text{v}$ calculate,
 - a) The value of R_B for operation in the saturated state
 - b) The value of R_B for an overdrive factor 5. [CO3,L3][10M]
 - c) Forced current gain and
 - d) Power loss in the transistor.

UNIT-II**RECTIFIERS**

- 1) Explain the operation of single phase half wave converter with R-load $\alpha=60^\circ$ with necessary waveforms. Also derive the output voltage, output current and RMS output voltages. [CO6,L3][10M]
- 2) Explain the operation of single phase Full wave converter with R-load with necessary waveforms. Also derive the output voltage, output current and RMS output voltages. [CO6,L2][10M]
- 3) a) List the different applications of phase controlled converters. [CO2,L2][5M]
b) What is the difference between half controlled and fully controlled bridge rectifier. [CO1,L5][5M]
- 4) A single phase half wave converter is operated from a 230V, 50Hz supply. If the load is Resistive of value 10 ohms and firing angle is 60° . Determine
i) the rectification efficiency
ii) form factor
iii) ripple factor
iv) Transformer utilization factor
v) Peak inverse voltage of thyristor. [CO6,L3][10M]
- 5) Analyze the average and RMS load voltage of single phase fully controlled rectifier with RL load. [CO6,L5][10M]
- 6) Explain the operation of Three phase fully controlled rectifier with RL load and also derive the average and RMS load voltage. [CO6,L2][10M]
- 7) Explain the operation of single phase half wave converter with RL Load with necessary wave forms. Also derive the output voltage, output current and RMS output voltages. [CO6,L2][10M]
- 8) Analyze the output voltage, output current & Rms voltage equations of single phase full Bridge converter with RL load. [CO6,L3][10M]
- 9) Explain the operation of Three phase fully controlled rectifier with R load and also derive the average and RMS load voltage. [CO6,L2][10M]
- 10) a) A single phase full converter is made to deliver a constant load current. For zero degree firing angle, the overlap angle is 15° , calculate the overlap angle when firing angle is a) 30° b) 45° and c) 60° [CO6,L3][5M]
b) What is the difference between half controlled and fully controlled bridge rectifier. [CO1,L2][5M]

UNIT-III
CHOPPERS

- 1) Derive the expression for output voltage of step down chopper with neat diagrams. [CO6,L2][10M]
- 2) a) Describe the principle of dc chopper operation. [CO2,L2][5M]
b) Derive an expression for its averaged output voltage. [CO5,L2][5M]
- 3) The buck converter has an input voltage of $E_{dc}=12V$. the required average output voltage is $E_0=5V$ At $R=500\Omega$ and the peak-to-peak output voltage is 20mV, the switching frequency is 25kHz. if the peak-to-peak ripple current of inductor is limited to 0.8A, determine
 - (a) the duty cycle
 - (b) the filter inductance L and
 - (c) the filter capacitor C , and
 - (d) the critical values of L and C . [CO5,L3][10M]
- 4) What is a dc chopper? Describe various types of chopper configurations. With appropriate diagram where necessary. [CO1,L4][10M]
- 5) Explain about Control Techniques of choppers in details. [CO5,L2][10M]
- 6) Explain the buck converter operation with help of diagram and also draw the output waveforms. [CO6,L2][10M]
- 7) Analyze elementary operation of chopper with waveforms. [CO5,L5][10M]
- 8) Explain the boost converter operation with help of diagram and also draw the output waveforms. [CO6,L2][10M]
- 9) The boost converter has an input voltage of $E_{dc}=5V$. the required average output voltage is $E_0=15V$ And the average load current $I_0=0.5A$. The switching frequency is 25 kHz. If the $L=150\mu H$ and $C=220\mu F$, Determine
 - (a) the duty cycle
 - (b) the ripple current of inductor ΔI
 - (c) the peak current of inductor I_2 ,
 - (d) The ripple voltage of filter capacitor ΔV_C , and
 - (e) the critical values of L and C . [CO5,L3][10M]
- 10) a) For step down chopper dc source voltage is 230v, load resistance is 10 ohm. The voltage drop across chopper when it is in ON is 2V. For a duty cycle of 0.4. Calculate
 - i) average and rms values of output voltage
 - ii) chopper efficiency. [CO5,L3][7M]
 b) List some applications of dc chopper? [CO1,L2][3M]

UNIT-IV**CYCLO CONVERTERS**

- 1) Explain the principle of operation of single phase to single phase step-up midpoint cycloconverter .
[CO2,L2][10M]
- 2) Explain the operation of single phase to single phase bridge type step-down cycloconverter with R-L Load for continuous conduction mode. [CO2,L2][10M]
- 3) a) What is meant by load commutated cycloconverter? [CO1,L2][10M]
b) Draw and explain bridge type step-down cycloconverter with R Load. [CO4,L4][10M]
- 4) The input voltage to the cycloconverter is 120V (r.m.s),50Hz. The load resister is 5Ω and the inductance is $L=40$ mH. The frequency of the output voltage is 25Hz. If the converters are operated as semiconverters such that $0 \leq \alpha \leq$ the delay angle is determine:
(a) The rms value of the output voltage.
(b) The rms value of the load current .(c) The input power factor. [CO4,L3][10M]
- 5) Explain the operation of single phase to single phase bridge type step-up cycloconverter with continues mode. [CO4,L2][10M]
- 6) Draw and explain bridge type step-up cycloconverter with R-L Load for discontinuous conduction mode. [CO4,L4][10M]
- 7) a) Draw and explain midpoint type step-down cycloconverter with R Load. [CO4,L4][10M]
b) What are the applications of cycloconverter. [CO1,L2][10M]
- 8) single-phase bridge-type cycloconverter has input voltage of 230V and 50Hz and load of $R = 10\Omega$. Output frequency is one-third of input frequency. For a firing angle delay of 300° , calculate
(a) RMS value of output voltage
(b) RMS current of each converter
(c) RMS current of each thyristor and
(d) input power factor. [CO4,L3][10M]
- 9) Explain the principle of operation of single phase to single phase step-down midpoint cycloconverter.
[CO6,L2][10M]
- 10) Draw and explain bridge type step-down cycloconverter with R-L Load for discontinuous conduction mode. [CO6,L4][10M]

UNIT-V

AC VOLTAGE CONTROLLERS

- 1) Explain the operation of single phase full wave ac voltage controller with resistive load. [CO6,L2][10M]
- 2) Draw and Explain the operation of single phase full wave ac voltage controller with R-L load. [CO6,L2][10M]
- 3) Briefly explain the operation of TRIAC in different modes. [CO6,L2][10M]
- 4) A single phase voltage controller is employed for controlling the power flow from 230V, 50Hz source into a load circuit consisting of $R=3\ \Omega$ and $L=4\ \Omega$. Calculate [CO4,L3][10M]
(i) the range of firing angle
(ii) the maximum value of rms load current
(iii) the maximum power and power factor
(iv) The maximum values of average and rms thyristor currents.
- 5) a) What is meant by ac voltage controllers and what are the different types? [CO2,L2][5M]
b) List the applications of ac voltage controller. [CO1,L2][5M]
- 6) Explain the operation of TRIAC with R and R-L loads. [CO4,L2][10M]
- 7) Explain about the single phase half wave ac voltage controller with resistive load. [CO4,L2][10M]
- 8) A single phase half wave ac voltage controller feeds a load of $R=20\ \Omega$ with an input voltage of 230V, 50Hz. Firing angle of thyristor is 45° . Determine
a) rms value of output voltage
b) power delivered to load and input pf and
c) average input current. [CO4,L3][10M]
- 9) a) Draw and Explain V-I Characteristics of TRIAC. [CO1,L4][6M]
b) What are the advantages and disadvantages of ac voltage controller? [CO1,L2][4M]
- 10) Explain the operation of TRIAC firing circuit. [CO2,L2][10M]

Prepared by: Dr. Chall Babu