



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR  
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code :** Basic Electrical Engineering(18EE0239)

**Course & Branch:** B.Tech–(ECE&CSE)

**Year & Sem:** I-B.Tech& II-Sem

**Regulation:** R18


**UNIT –I  
DC CIRCUITS**

1. (a) State and explain Kirchhoff's laws?

[L1][4M]

(b) Determine the current in branch A-B by using KVL

[L4][6M]

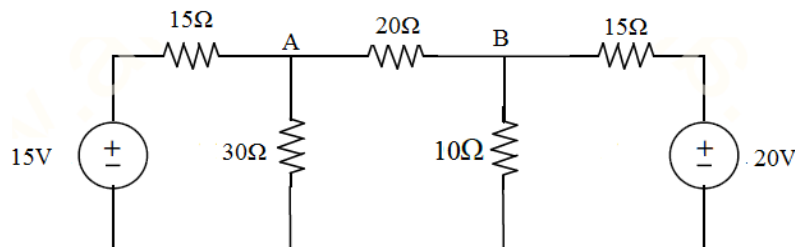


2. a) State and explain Norton's theorem?

[L1] [5M]


b) Draw the Norton's equivalent circuit for the circuit shown in figure.

[L4] [5M]

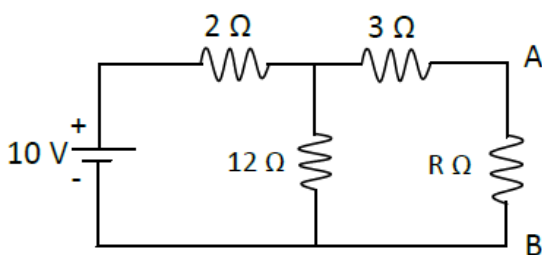


3. Determine the mesh currents for the circuit shown below.

[L4] [10M]

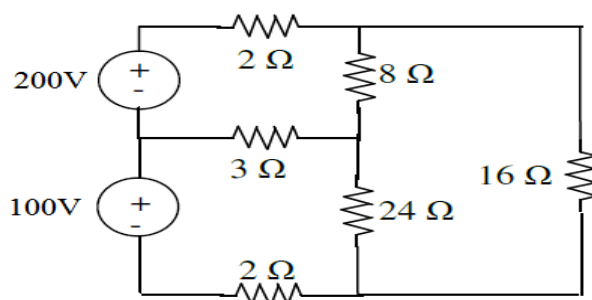


4. Use nodal analysis to find the node voltages for the below circuit.

[L4] [10M]

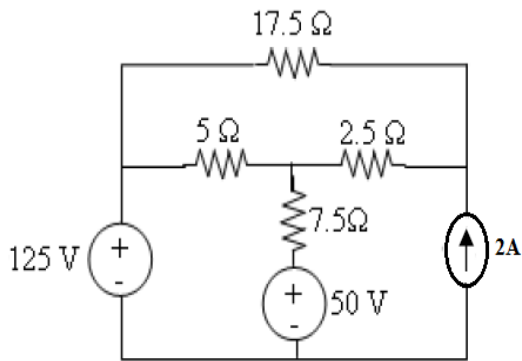


5. a) State and Explain Thevenin's Theorem [L1] [5M]

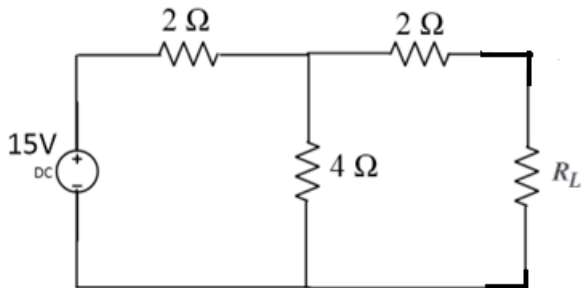b) Find load current by using Thevenin's theorem for the following circuit where  $R_L=3\Omega$  [L4] [6M]




6 a) Derive the time response of RL circuit [L2] [5M]

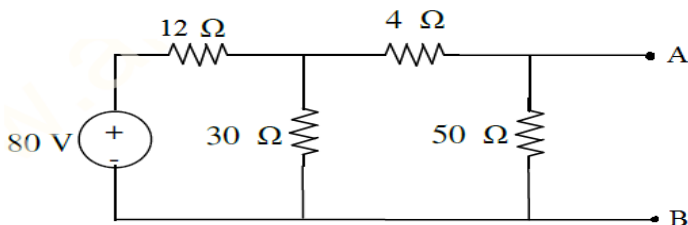b) find the Thevenin's equivalent for the circuit shown below [L4] [5M]




7. a) Derive the time response of RC circuit [L2] [5M]

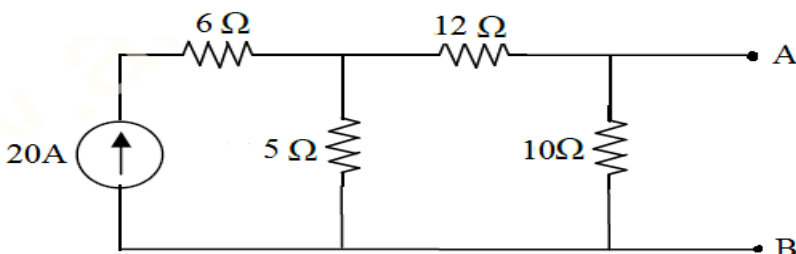b) find the Norton's equivalent for the circuit shown below. [L4] [5M]



8.a) State and explain Superposition theorem? [L1] [4M]

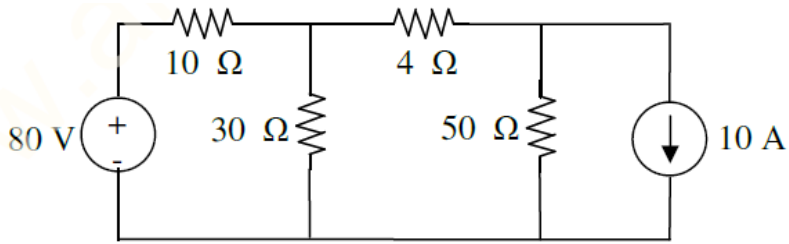b) Verify Superposition theorem for 4Ω resistor for the following circuit. [L4] [6M]




9. a) explain the circuit elements R,L &C.

[L1] [4M]

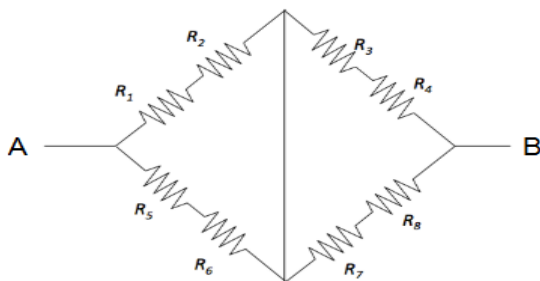b) i) Find the equivalent resistance between AB for the circuit shown below.


[L3] [3M]

$R_1=4\Omega$ ,  $R_2=2\Omega$ ,  $R_3=8\Omega$ ,  $R_4=1\Omega$ ,  $R_5=12\Omega$ ,  $R_6=3\Omega$ ,  $R_7=10\Omega$  &  $R_8=5\Omega$




ii) Find the equivalent resistance for the circuit shown below.

[L3] [3M]

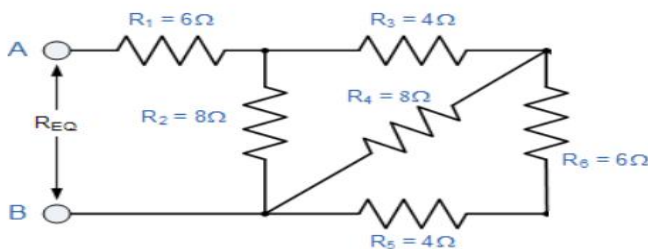

10. State and Explain the Superposition theorem. And By using superposition theorem find the current flowing through the 3 ohm resistor.

[L4] [10M]

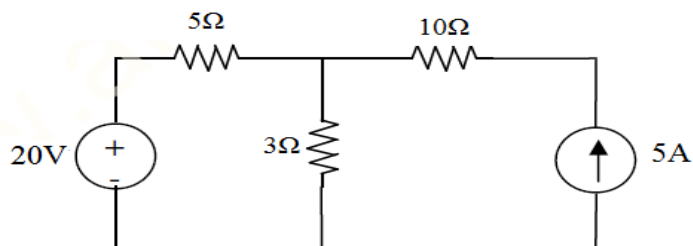



- 11.(a) What is Circuit and Network? [L1][2M]  
 (b) Define Inductance ? [L1][2M]  
 (c) Define Capacitor and represent symbolically ? [L1][2M]  
 (d) State Ohm's law and write its expression ? [L1][2M]  
 (e) A electric kettle takes a current of 12.5A at 240V. What is the resistance of heating Element ? [L1][2M]

## UNIT-II

### AC CIRCUITS

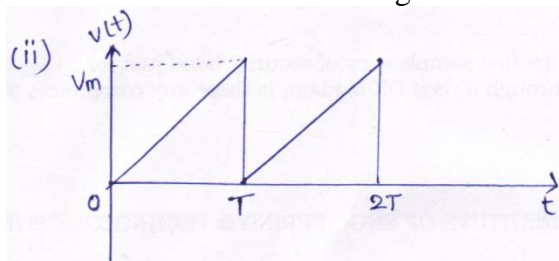1. (a) Derive an expression for RMS values of sine wave form. [L2][6M]  
 (b) An alternating current is expressed as  $I = 14.14 \sin 314t$ . Determine. [L4][4M]  
 i. Maximum current    ii. rms current    iii. Frequency  
 iv. Instantaneous current when  $t = 0.02\text{msec}$ .
2. Derive an expression for the current and impedance for a series RL and RC circuit excited by a sinusoidally alternating voltage. Draw the phasor diagrams. [L3][10M]
3. a) Define Admittance and impedance [L1][4M]  
 b) The impedances of series circuit are  $Z_1 = (6+j8)$  ohms and  $Z_2 = (8-j6)$  ohms. If the applied voltage is 120V, find total impedance, current and power factor. Draw the phasor diagram. [L2] [6M]
4. (a) Explain parallel RL and RC circuits with phasor diagrams. [L3][6M]  
 (b) A 120V AC circuit contain  $10 \Omega$  resistance and  $30 \Omega$  inductive reactance in series. What is average power of this circuit. [L2][4M]
5. (a) Define power factor, apparent power, active power and reactive power [L1] [4M]  
 (b)  $Z_1$  and  $Z_2$  are in parallel where currents corresponding impedances are  $I_1 = 50 \angle 10$  and  $I_2 = 20 \angle 30$ . If the applied voltage is  $100 \angle 15^\circ$  V, find true power, reactive power and apparent power in each branch. [L2] [6M]
6. a) Derive an expression for the voltage and impedance for a series RLC circuit excited by a sinusoidally alternating voltage. [L2] [5M]  
 (b) A series circuit consisting of a  $10 \Omega$  resistor, a  $100 \mu\text{F}$  capacitor and a  $10 \text{ mH}$  inductor is driven by a  $50 \text{ Hz}$  a.c. voltage source of maximum value 100 volts. Calculate the equivalent impedance, Current in the circuit and the phase angle. [L2] [5M]
7. (a) Derive the voltage and current relations in three phase balanced circuits for delta connection. [L2] [6M]  
 (b) Find the rms value for the following waveform [L3] [4M]



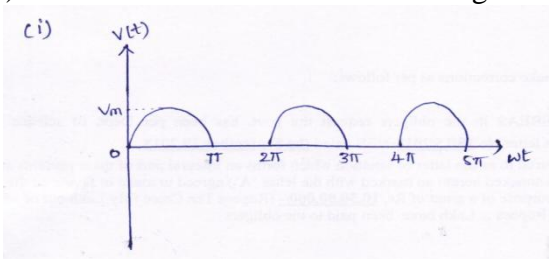8. (a) Explain the phasor relation for R, L & C elements. [L1][4M]
- (b) A resistor of  $50\Omega$  and inductance of  $100\text{mH}$  are connected in series across  $200\text{V}$ ,  $50\text{Hz}$  supply. Determine the following [L2] [6M]
- (i) Impedance (ii) current flowing through the circuit (iii) power factor
9. (a) Derive the voltage and current relations in three phase balanced circuits for star connection. [L2] [10M]
- (b) Find the rms value for the following waveforms [L3] [4M]
- (c i)
- 
10. (a) Explain resonance for series RLC circuit and derive the equation for resonant frequency. [L2] [5M]
- (b) A series RLC circuit of  $R=50\text{ ohms}$ ,  $L= j25\text{ ohms}$ . Determine the value of capacitive reactance and impedance at resonance [L2] [5M]
11. (a) Define Form Factor and Peak Factor? [L1][2M]
- (b) Define vector and phasor? [L1][2M]
- (c) Define resonance? [L1][2M]
- (d) Draw Star and Delta Connections of Three Phase circuit? [L1][2M]
- (e) Write Expressions for Voltages and Current in Three Phase balanced system? [L1][2M]

### Unit-III

### TRANSFORMERS

- 1.(a) Explain the briefly the construction and working of a single phase transformer [L2][6M]
- (b) A  $200\text{ KVA}$ ,  $1100/415\text{V}$ ,  $50\text{Hz}$  single phase transformer has  $80$  turns of secondary. Calculate the primary number of turns. [L2][4M]
- 2.(a)Write a short notes on regulation and Efficiency of the transformer. [L1][5M]
- (b)The efficiency of a  $200\text{ KVA}$ ,  $1-\Phi$  transformer is  $98.7\%$  when operating at full-load,  $0.8\text{ p.f}$  lagging, the iron loss in the transformer is  $200\text{ W}$ . Calculate: (i)Full load copper loss (ii) Half load copper loss. [L3][5M]
3. (a)Explain the various losses in a transformer. [L1][5M]

- (b) a single phase transformer with a ratio of 440/110V takes a no load current of 5A at 0.2 p.f. lagging. If the secondary supplies a current of 120A at a p.f. of 0.8 lagging. find the current taken by the primary. [L3] [5M]
4. (a) Explain BH characteristics. [L1] [5M]
- (b) A 100KVA transformer has primary and secondary turns of 400 and 100 respectively. Its primary and secondary resistance and reactance are:  $R_1=0.3\Omega$ ,  $R_2=0.015\Omega$ ,  $X_1=1.1\Omega$ ,  $X_2=0.055\Omega$ , supply voltage is 2400V. Calculate equivalent resistance and reactance on the primary side. [L2] [5M]
5. (a) Explain about magnetic materials. [L1] [4M]
- (b) A 1- $\Phi$ , 50 HZ transformer has 80 turns on the primary winding and 400 turns on the secondary winding. The net cross sectional area of the core is  $200\text{ cm}^2$ . If the primary winding is connected to a 240V, 50 HZ supply, determine (i) The emf induced in the secondary winding.
- (ii) The maximum value of the flux density in the core. [L2] [6M]
6. (a) Explain about ideal transformer and derive the EMF equation of the transformer. [L2] [6M]
- (b) A 10KVA, 2200/220V, 50Hz single phase transformer has a net core area of  $300\text{ cm}^2$  and a maximum flux density of  $1.5\text{ wb/m}^2$ . Calculate the number of turns in primary and secondary winding. [L2] [6M]
7. Explain the practical transformer on load and draw the phasor diagrams. [L2] [10M]
8. Obtain the equivalent circuit of single phase transformer referred to primary and secondary. [L2] [10M]
9. What is meant by auto transformer? What are the advantages of Auto transformer when compared to two winding transformer? [L1] [10M]
10. What are three phase transformer connections and explain it? [L2] [10M]
11. (a) Define Transformer? [L1] [2M]
- (b) Write Transformation ratio? [L1] [2M]
- (c) Why Transformer doesn't work on DC? [L1] [2M]
- (d) Why Transformer rating will be in kVA? [L1] [2M]
- (e) What is the condition for maximum efficiency in a Transformer and expression for load current at maximum efficiency? [L1] [2M]

**Unit-IV****ELECTRICAL MACHINES**

1. What is rotating magnetic field? Explain in brief? [L2][10M]
2. Explain the construction of three phase induction motor? [L1][10M]
3. Sketch and explain the torque slip characteristics of 3 phase induction motor? [L2][10M]
4. Explain the construction of three phase alternator? [L1][10M]
5. Explain the construction single phase induction motor [L1][10M]
6. Explain the working principle of single phase induction motor [L2][10M]
7. Explain the construction of DC motor? [L1][10M]
8. Sketch and explain the torque speed characteristics of DC motor? [L2][10M]
9. Explain the various method of speed control of separately excited DC motor? [L2][10M]
10. Explain the working principle of synchronous generator? [L2][10M]
11. (a) Define Torque and slip? [L1][2M]
- (b) Why is an induction motor called a rotating transformer? justify [L1][2M]
- (c) why single phase induction motor is not self starting? [L1][2M]
- (d) What is commutation & commutator? [L1][2M]
- (e) Define Alternator ? [L1][2M]

**UNIT -V****ELECTRICAL INSTALLATIONS**

1. Explain different types of wiring system. [L2][10M]
2. Explain the following electrical wiring system with necessary diagrams. [L2][10M]
- (a) CTS wiring and (b) Concealed wiring
3. With relevant diagrams explain in detail about various types of fuses used in electrical wiring systems. [L2][10M]
4. Explain briefly about earthing and how it plays an important role in installation. [L2][10M]
5. a) How many types of batteries are there? [L1][5M]
- b) Explain the characteristics of batteries. [L2][5M]
6. Explain different methods used for improvement of power factor. [L2][10M]
7. a) Explain battery backup. [L1][5M]
- b) How many types of cables are there? Explain them with neat sketch. [L1][5M]
8. What is energy consumption and Explain how it is calculated by an example. [L2][10M]
9. a) What is the importance of wiring. [L2][5M]
- b) Explain how wiring system is classified. [L2][5M]
10. Explain about [L2][10M]
- a) pvc cables and b) wheather proof cables
11. (a) Define Switch Gear? [L1][2M]
- (b) Define Battery? [L1][2M]
- (c) Define Energy and write it's expression? [L1][2M]
- (d) Define Fuse and Circuit Breaker? [L1][2M]
- (e) What is Earthing? [L1][2M]